

REAR56958B

Voltage Detecting, System Resetting IC Series

DESCRIPTION

REAR56958B is the semiconductor integrated circuit for resetting of all types of logic circuits such as CPUs, and has the feature of setting the detection voltage by adding external resistance.


They include a built-in delay circuit to provide the desired retardation time simply by adding an external capacitor.

They found extensive applications, including battery checking circuit, level detecting circuit and waveform shaping circuit.

FEATURES

- Few external parts
- Large delay time with a capacitor of small capacitance ($t_d \approx 100\text{ms}$, at $0.33\mu\text{F}$)
- Wide supply voltage range: 2V to 17V
- Wide application range


PRODUCT LINEUP

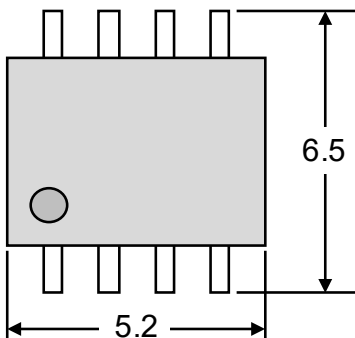Package Type	SOP
Part Name	REAR56958BGSM
Outline	Unit : mm 


ORDERING INFORMATION

Order Name	Quality Level	Package
REAR56958BGSM#HCA	Normal Quality Level	8-Pin plastic SOP (5.72 mm (225))


Pin Arrangement

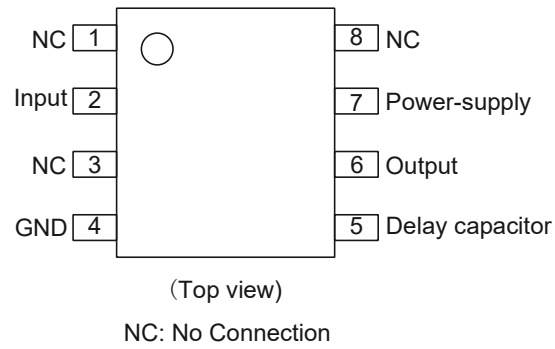

Block Diagram

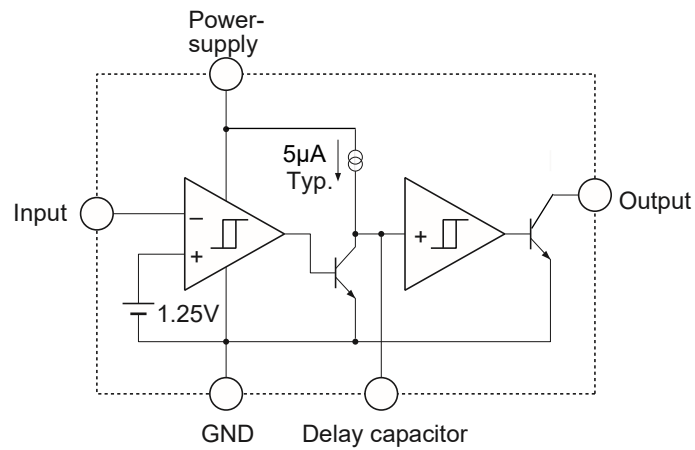

Operating Waveform

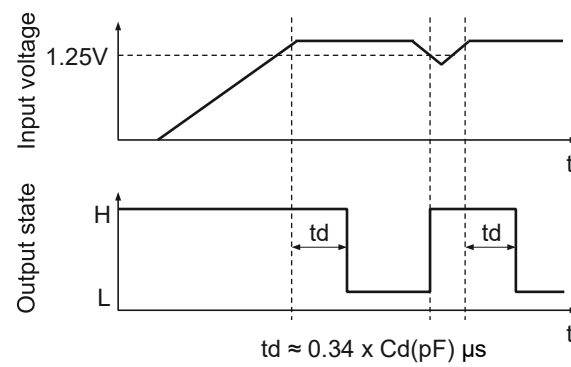

ABSOLUTE MAXIMUM RATINGS(T_a = 25°C, unless otherwise noted)

Item	Symbol	Ratings	Unit	Conditions
Supply Voltage	V _{CC}	-0.3 to +18	V	
Output Sink Current	I _{SINK}	6	mA	
Output Applied Voltage	V _O	-0.3 to +18	V	Type B (open collector output)
Total Power Dissipation	P _d	440	mW	
Thermal Derating	K _θ	4.4	mW/°C	Refer to the thermal derating curve.
Operating Temperature	T _{opr}	-40 to +85	°C	
Storage temperature	T _{stg}	-55 to +125	°C	
Input Voltage Range	V _{IN}	-0.3 to V _{CC}	V	V _{CC} ≤ 7V
		-0.3 to +7		V _{CC} > 7V

RECOMMENDED OPERATING CONDITION

Item	Symbol	MIN.	TYP.	MAX.	Unit
Supply Voltage	V _{CC}	2		17	V







ELECTRICAL CHARACTERISTICS(T_a = 25°C, unless otherwise noted)




“H” Reset Type

Item	Symbol	Min.	Typ.	Max.	Unit	Test Conditions
Detecting Voltage	V _S	1.20	1.25	1.30	V	
Hysteresis Voltage	ΔV _S	9	15	23	mV	V _{CC} = 5V
Detecting Voltage Temperature Coefficient	V _S /ΔT		0.01		%/°C	
Supply Voltage Range	V _{CC}	2		17	V	
Input Voltage Range	V _{IN}	-0.3		V _{CC}	V	V _{CC} ≤ 7V
		-0.3		7.0		V _{CC} > 7V
Input Current	I _{IN}		100	500	nA	V _{IN} = 1.25V
Circuit Current	I _{CC}		360	540	μA	Type B, V _{CC} = 5V
Delay Time	T _{pd}	1.6	3.4	7.0	ms	C _d = 0.01μF ^{Note.1}
Constant Current	I _{pd}	-8	-5	-3	μA	V _{CC} = 5V
Output Saturation Voltage	V _{sat}		0.2	0.4	V	V _{CC} = 5V, V _{IN} > 1.35V, I _{SINK} = 4mA
Output Leakage Current	I _{OH}			30	nA	Type B, V _{out} ≤ 17V

【Note】 1. Please set the desired delay time by attaching capacitor of the range between 4700pF and 10μF.

TYPICAL CHARACTERISTICS

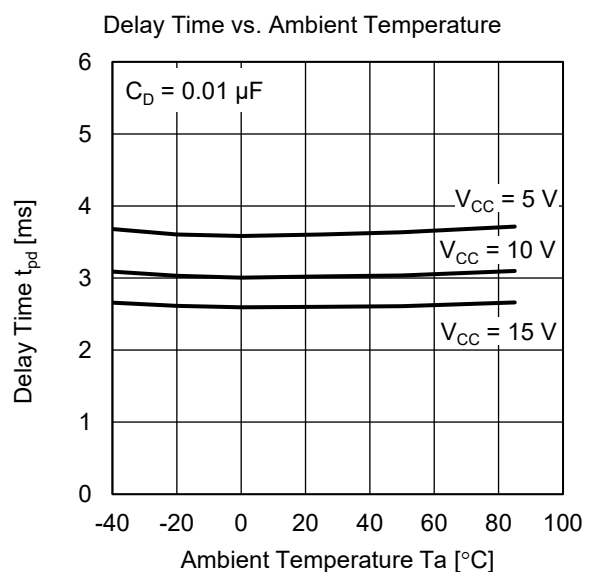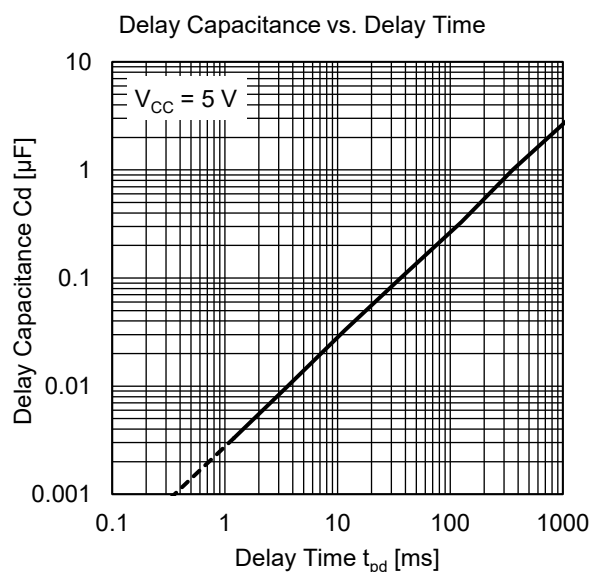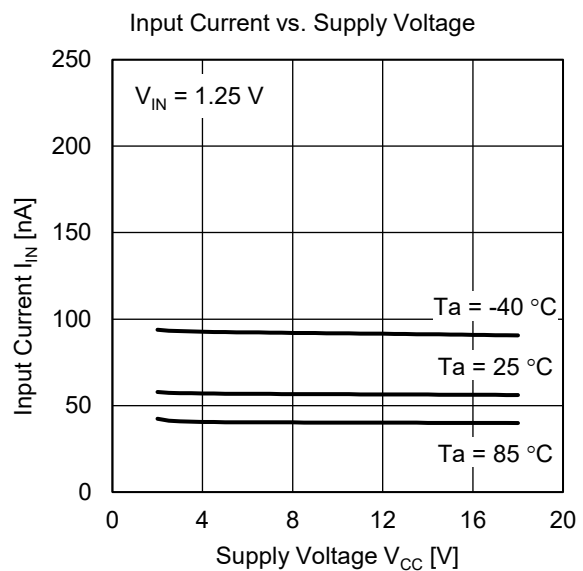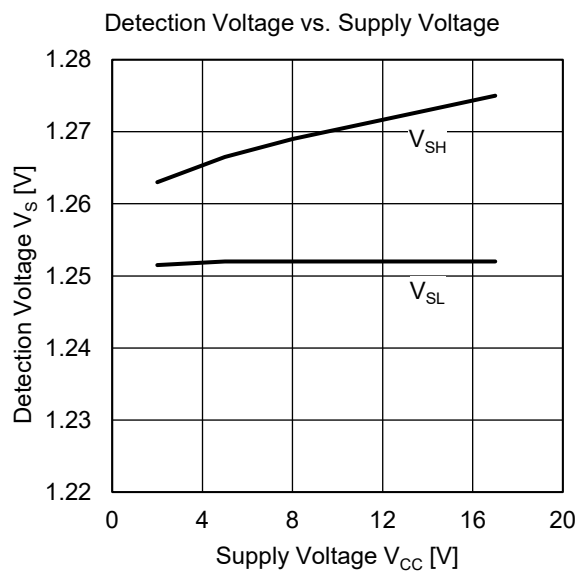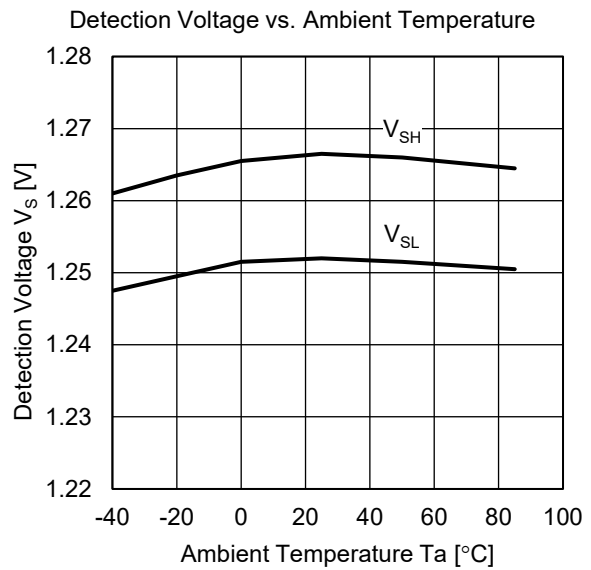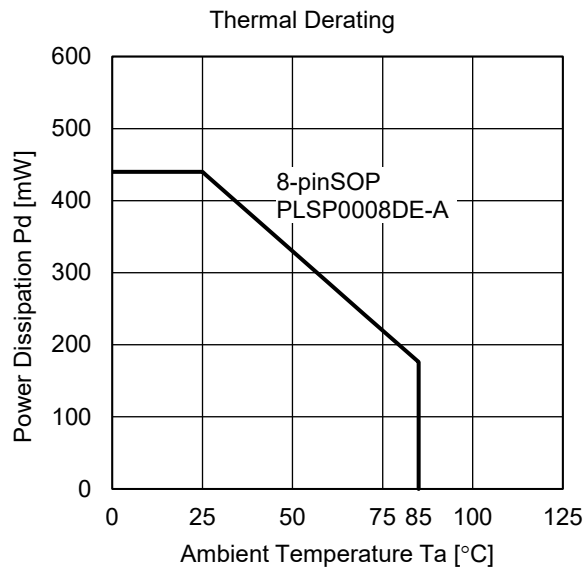


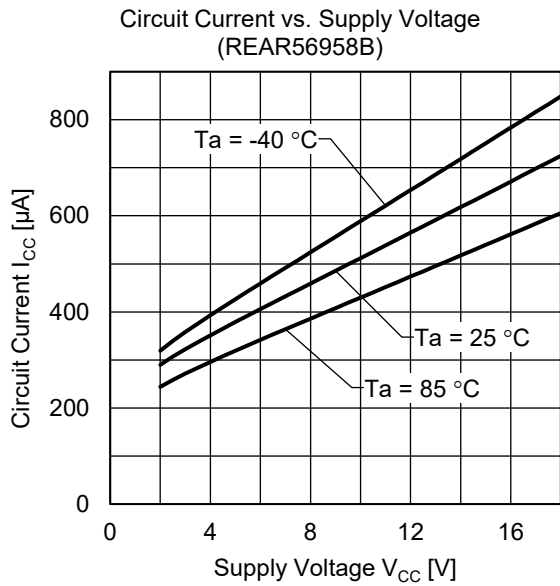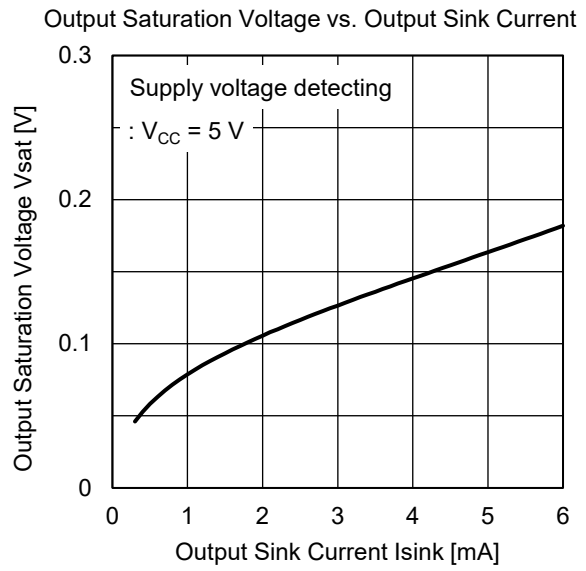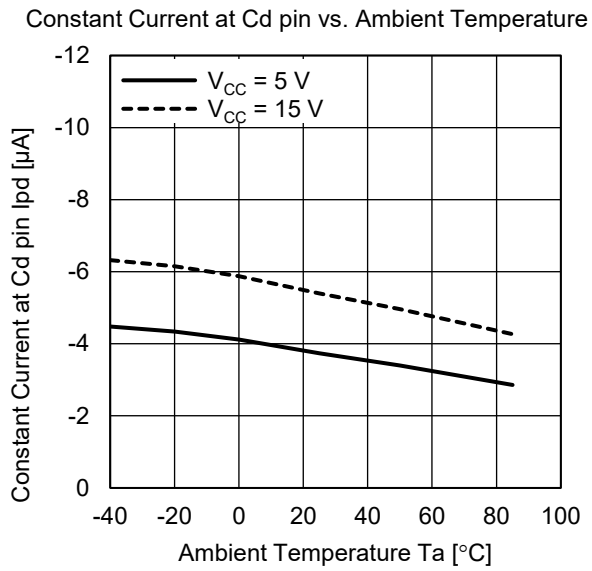

PACKAGE DRAWINGS

8-PIN PLASTIC SOP

JEITA Package code	RENESAS code	MASS (TYP.) [g]
P-LSOP8-4.4×5.2-1.27	PLSP0008DE-A	0.09[g]

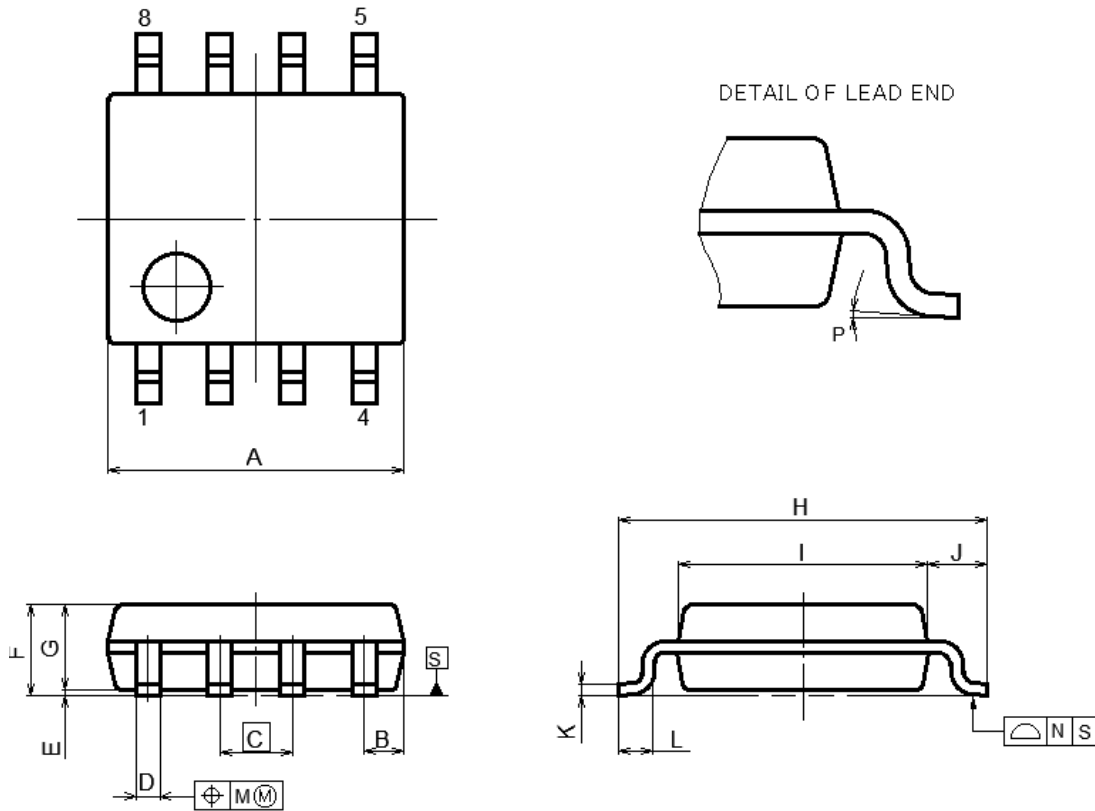

NOTE


EACH LEAD CENTERLINE IS LOCATED WITHIN 0.12 MM OF ITS TRUE POSITION(T.P.) AT MAXIMUM MATERIAL CONDITION.

(UNIT:mm)

ITEM	DIMENSIONS
A	5.2±0.17
B	0.78MAX
C	1.27(T.P)
D	0.40±0.05
E	0.1±0.1
F	1.59±0.21
G	1.49
H	6.5±0.3
I	4.4±0.1
J	1.05±0.15
K	0.2±0.07
L	0.6±0.20
M	0.1MAX
N	0.1MAX
P	4°±4°

EXAMPLE OF APPLICATION CIRCUIT

Reset Circuit of REAR56958B

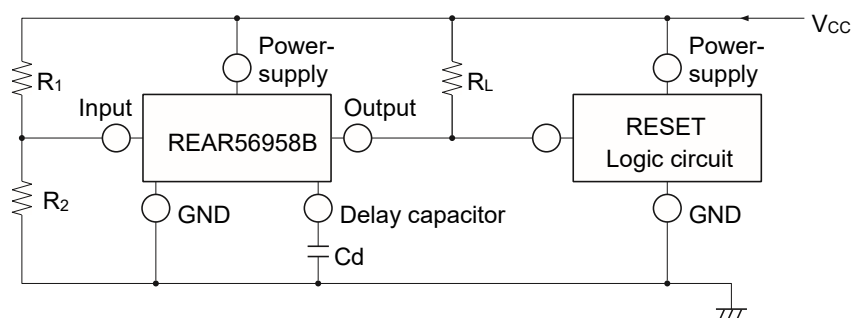

Reset Circuit of REAR56958B


- Notes :
1. The detecting supply voltage is $V_s \times (R_1 + R_2)/R_2$ (V) approximately. $V_s = 1.25$ V (Typ.)
The detecting supply voltage can be set between 2 V and 15 V
 2. The delay time is about $0.34 \times C_d$ (pF) μ s.
 3. The logic circuit preferably should not have a pull-down resistor, but if one is present, add load resistor R_L to overcome the pull-down resistor.
 4. When a negative supply voltage is used, the supply voltage side of REAR56958B and the GND side are connected to negative supply voltage respectively.

Application Example on 3V Microcontroller System

The input voltage detection type can be used for voltage monitoring of 3V microcontroller system as shown on Figure .


The constant in Figure sets the detection voltage to 2.66V (TYP.). However, the detection voltage can be adjusted by changing R_1 or R_2 .

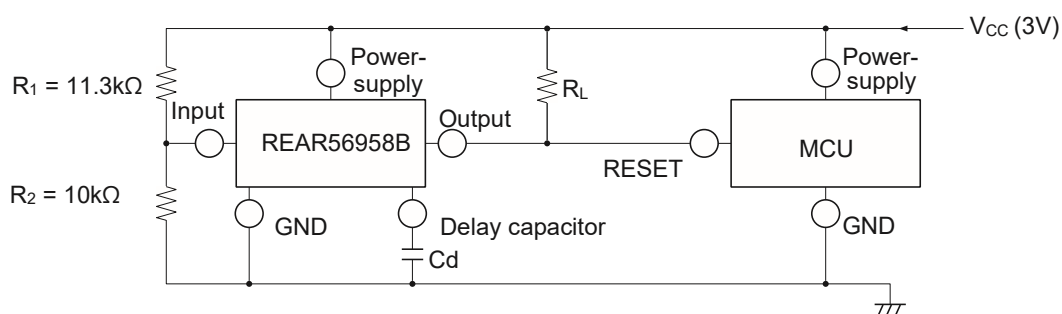The detection accuracy of the IC alone is $\pm 4\%$.



Application Example on 3V Microcontroller System

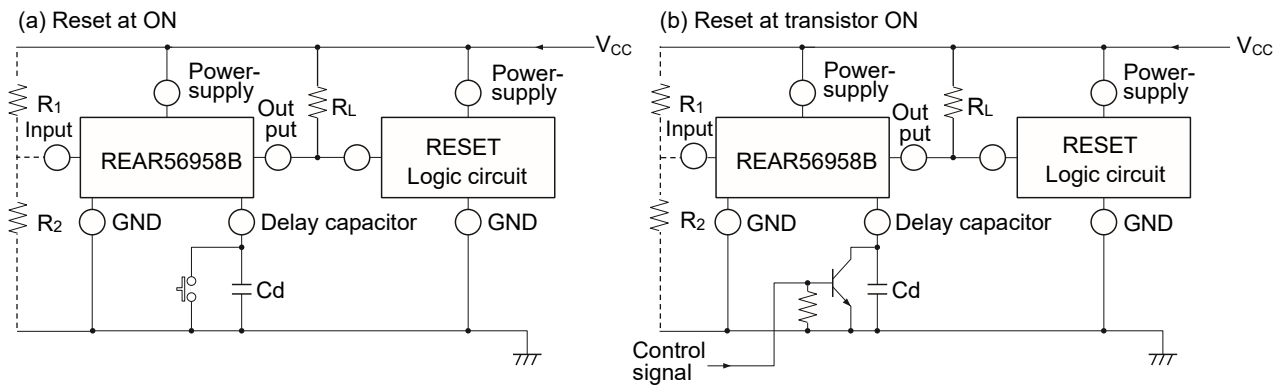
Case of Using Reset Signal except Supply Voltage in the REAR56958B



Case of Using Reset Signal except Supply Voltage in the REAR56958B


Delay Waveform Generating Circuit

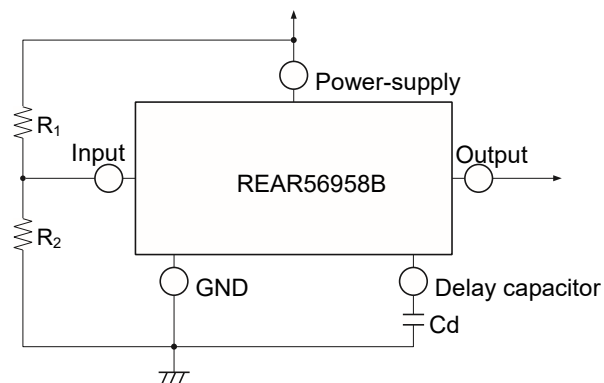When REAR56958B are used, a waveform with a large delay time can generate only by adding a small capacitor.



Delay Waveform Generating Circuit

Operating Waveform

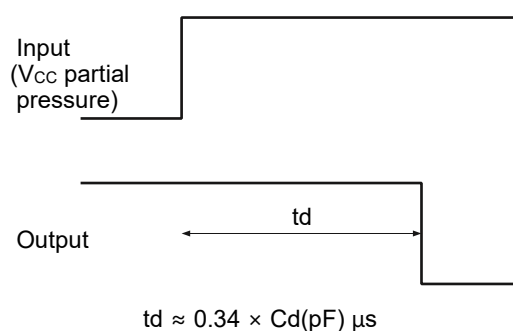

Operating Waveform


NOTICE FOR USE

About the Power Supply Line

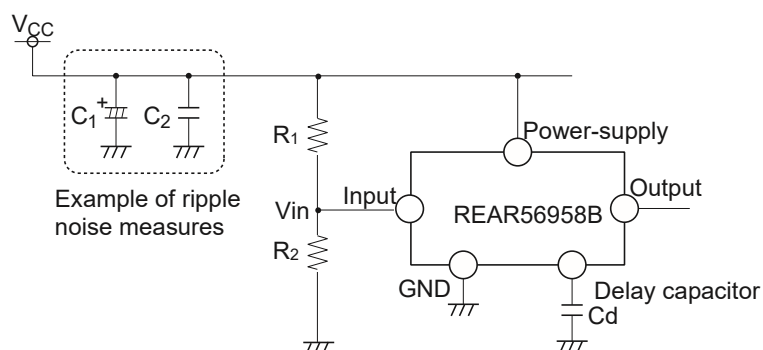1. About bypass capacitor

Because the ripple and the spike of the high frequency noise and the low frequency are superimposed to the power supply line, it is necessary to remove these.

Therefore, please install C_1 and C_2 for the low frequency and for the high frequency between the power supply line and the GND line as shown in following figure.



Example of Ripple Noise Measures

2. The sequence of voltage impression

Please do not impress the voltages to the input terminals earlier than the power supply terminal.

Moreover, please do not open the power supply terminal with the voltage impressed to the input terminal. (The setting of the bias of an internal circuit collapses, and a parasitic element might operate.)

About the Input Terminal

1. Setting range of input voltage


The following voltage is recommended to be input to the input terminal (pin 2).

about $0.8\text{ (V)} < V_{in} < V_{CC} - 0.3\text{ (V)}$... at $V_{CC} \leq 7\text{ V}$


about $0.8\text{ (V)} < V_{in} < 6.7\text{ (V)}$ at $V_{CC} > 7\text{ V}$

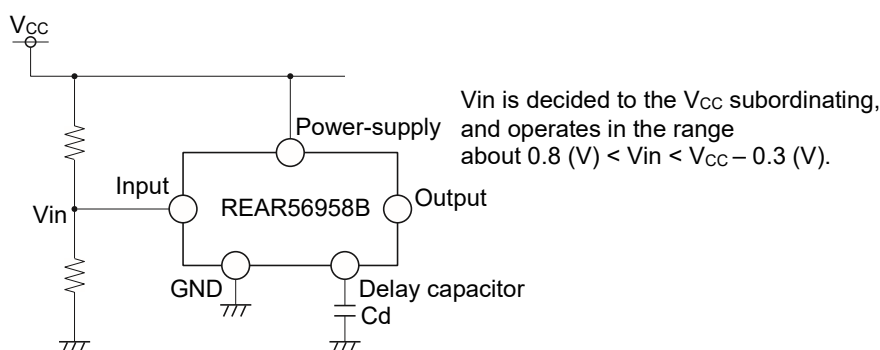2. About using input terminal


Please do an enough verification to the transition characteristic etc. of the power supply when using independent power supply to input terminal (pin 2).



Recommended Example of Circuit

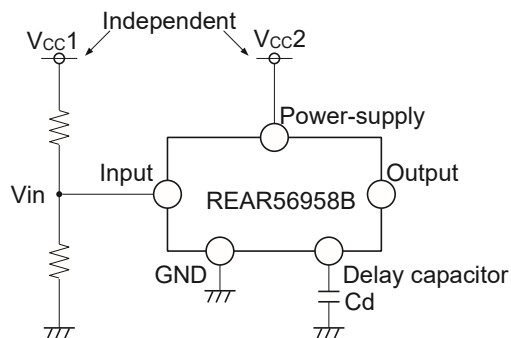

Example 1. Independent power supply system
Please do enough verifying about transition characteristic of V_{CC1} and V_{CC2}.

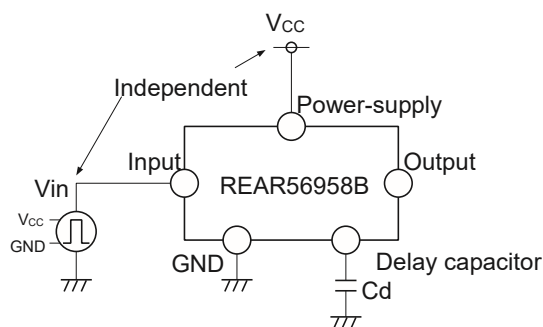

Example 2. Logic pulse input
(not recommended)


3. Calculation of detecting voltage

Detecting voltage V_s can be calculated by the following expression.

However, the error margin is caused in the detecting voltage because input current I_{in} (standard 100 nA) exists if it sets too big resistance.

Please set the constant to disregard this error margin.
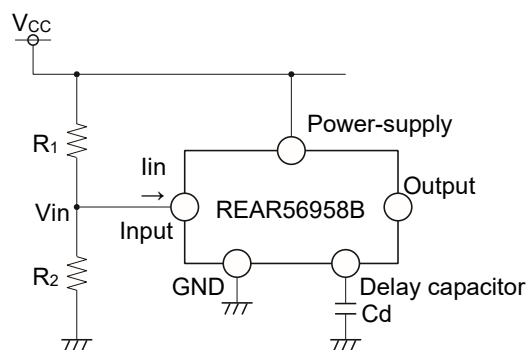
$$V_s = 1.25 \times \left(\frac{R_1 + R_2}{R_2} \right) + \frac{I_{in} \times R_1}{\text{error margin}}$$



Influence of Input Current

4. About the voltage input outside ratings


Please do not input the voltage outside ratings to the input terminal.

An internal protection diode becomes order bias, and a large current flows.

Setting of Delay Capacity

Please use capacitor C_d for the delay within the range of 10 μF or less.

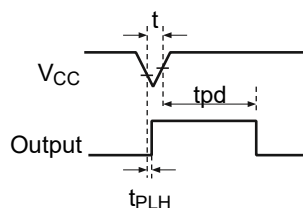When a value that is bigger than this is set, the problem such as following (1), (2), and (3) becomes remarkable.



Time Chart at Momentary Voltage-Decrease

(1) The difference at delay time becomes remarkable.

A long delay setting of tens of seconds is fundamentally possible. However, when set delay time is lengthened, the range of the difference relatively grows, too. When a set value is assumed to be 'tpd', the difference occurs in the range from $0.47 \times \text{tpd}$ to $2.05 \times \text{tpd}$. For instance, 34 seconds can be calculated at 100 μF . However, it is likely to vary within the ranges of 16-70 seconds.

(2) Difficulty to react to a momentary voltage decrease.

For example, the reaction time t_{PLH} is 10 μs when delay capacitor $C_d = 0.1 \mu\text{F}$.

The momentary voltage-decrease that is longer than such t_{PLH} occurs, the detection becomes possible. When the delay capacitance is enlarged, t_{PLH} also becomes long. For instance, it becomes about 100 to 200 μs in case of circuit constant $C_1 = 100 \mu\text{F}$.



(Characteristic graph 1 is used and extrapolation in case of $C_d = 100 \mu\text{F}$.)

Therefore, it doesn't react to momentary voltage-decrease that is shorter than this.

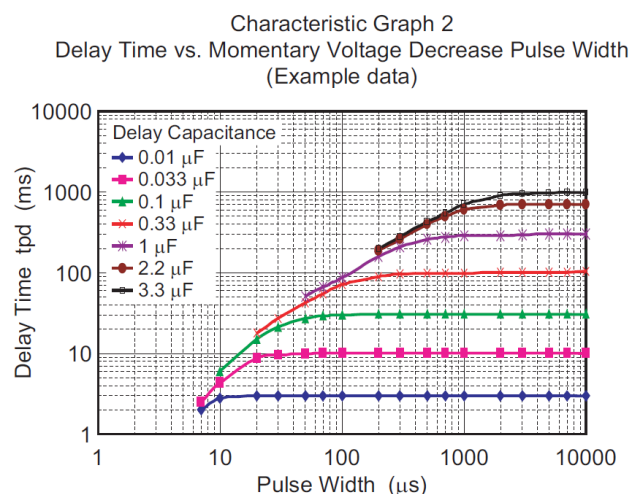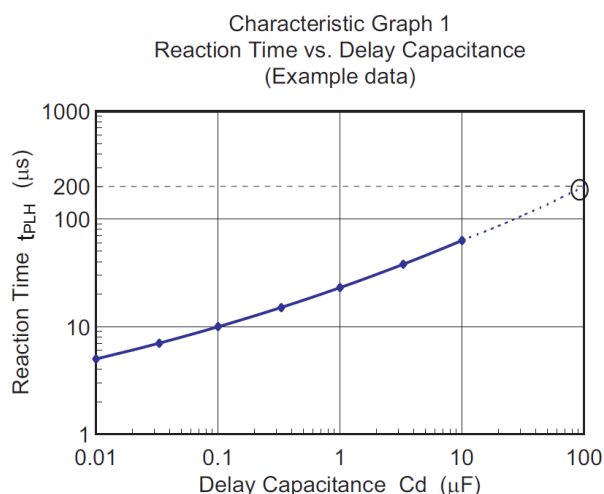(3) Original delay time is not obtained.

When the momentary voltage-decrease time 't' is equivalent to t_{PLH} , the discharge becomes insufficient and the charge starts at that state. This phenomenon occurs at large capacitance. And, original delay time tpd is not obtained.

Please refer to characteristic graph 2. (Delay time versus input pulse width)




Characteristic Graph

Setting of Output Load Resistance (REAR56958B)

High level output voltage can be set without depending on the power-supply voltage because the output terminal is an open collector type. However, please guard the following notes.

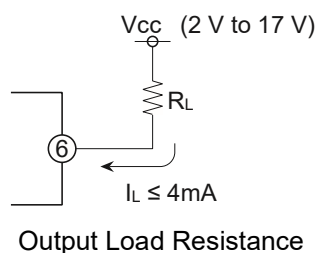1. Please set it in value (2 V to 17 V) within the range of the power-supply voltage recommendation. Moreover, please never impress the voltage of maximum ratings 18 V or more even momentarily either.
2. Please set output load resistance (pull-up resistance) R_L so that the output current (output inflow current I_L) at L level may become 4 mA or less. Moreover, please never exceed absolute maximum rating (6 mA).



Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.

7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.5.0-1 October 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/